
 


(I) Layout with ruler:

 
1.4-bit carry-ripple adder: $40.47 \times 7.99 = 323.3553$




2.4-bit carry-skip adder: $40.74 \times 13.06 = 532.0644$



3.4:1 MUX: $12.87 \times 4.83 = 62.1621$

 


 
4.Dynamic inverter: $3.04 \times 2.72 = 8.2688$




(ii) Postsim waveform

 
1. 4-bit carry-ripple adder (cin to cout delay: 607.78p)



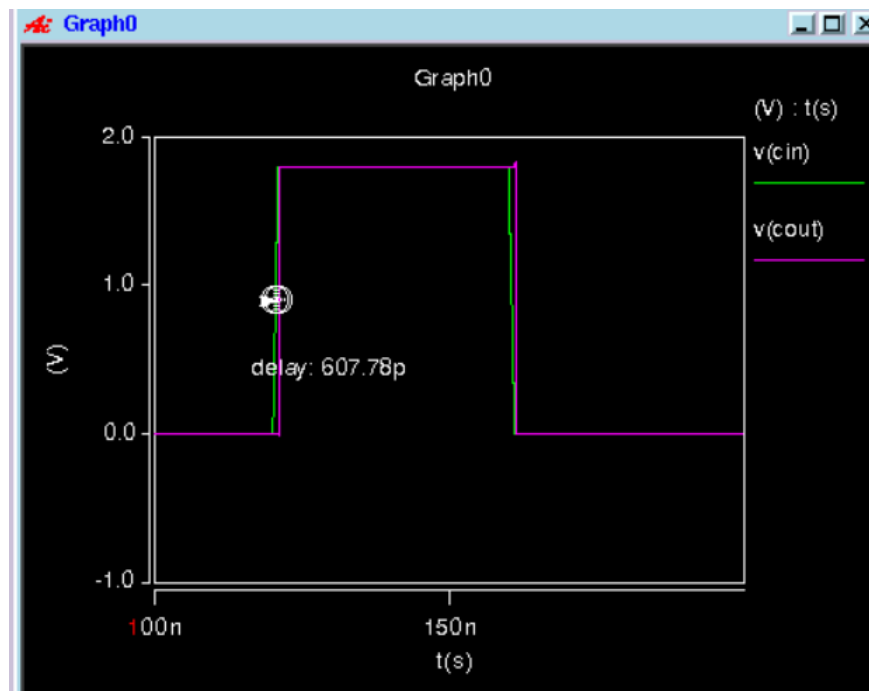


 
2. 4-bit carry-skip adder(cin to cout delay:647.74p)



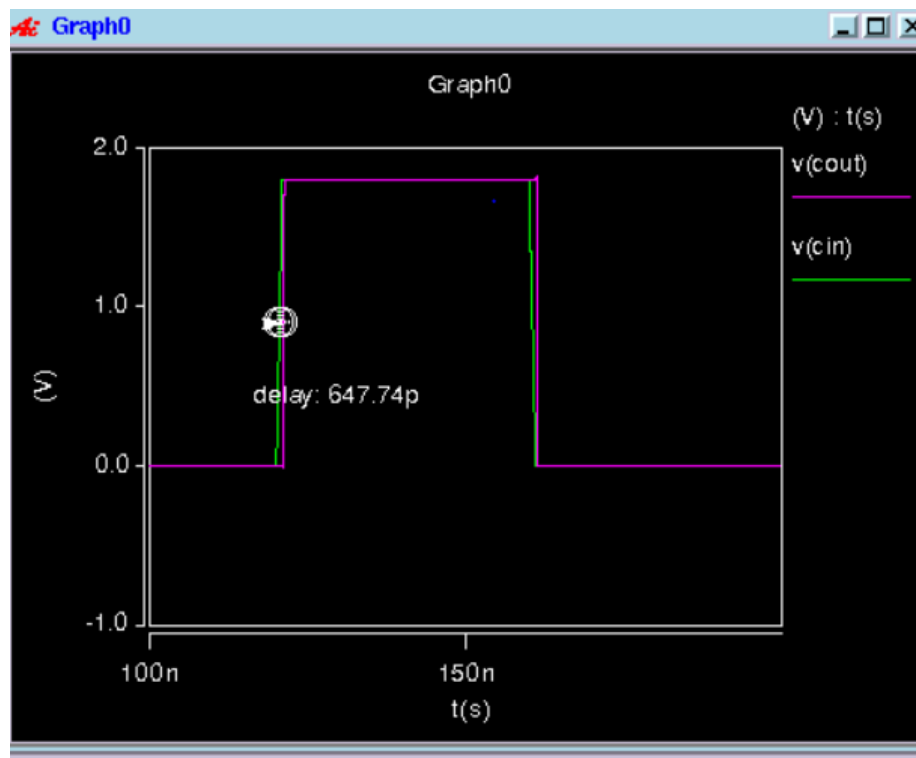



3. 4:1 MUX(DelayD0_b to Y:169.31p)

 

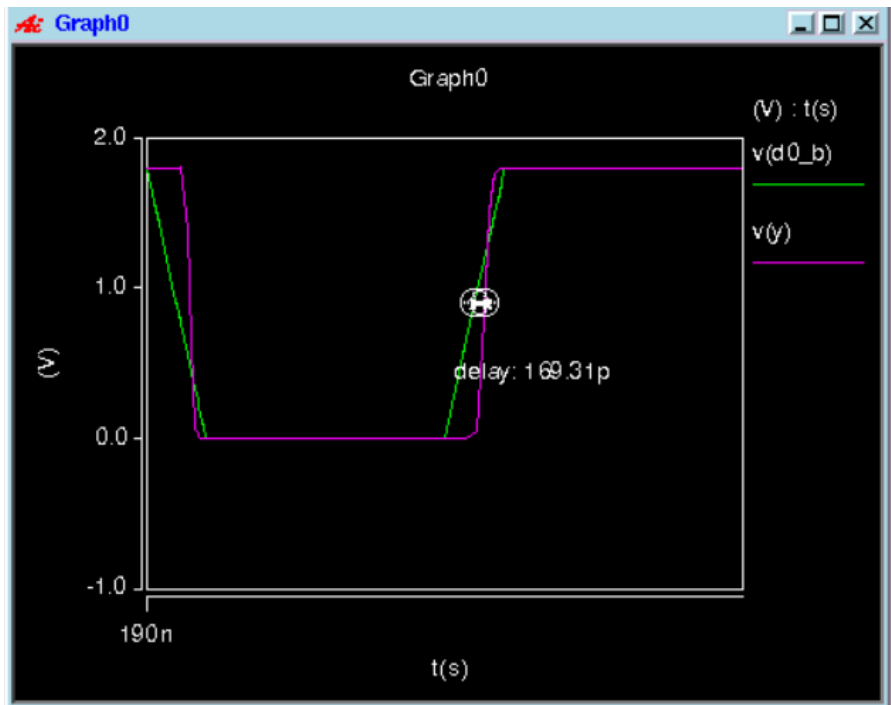

4. Dynamic inverter(DelayΦ to Y:22.571p)

 

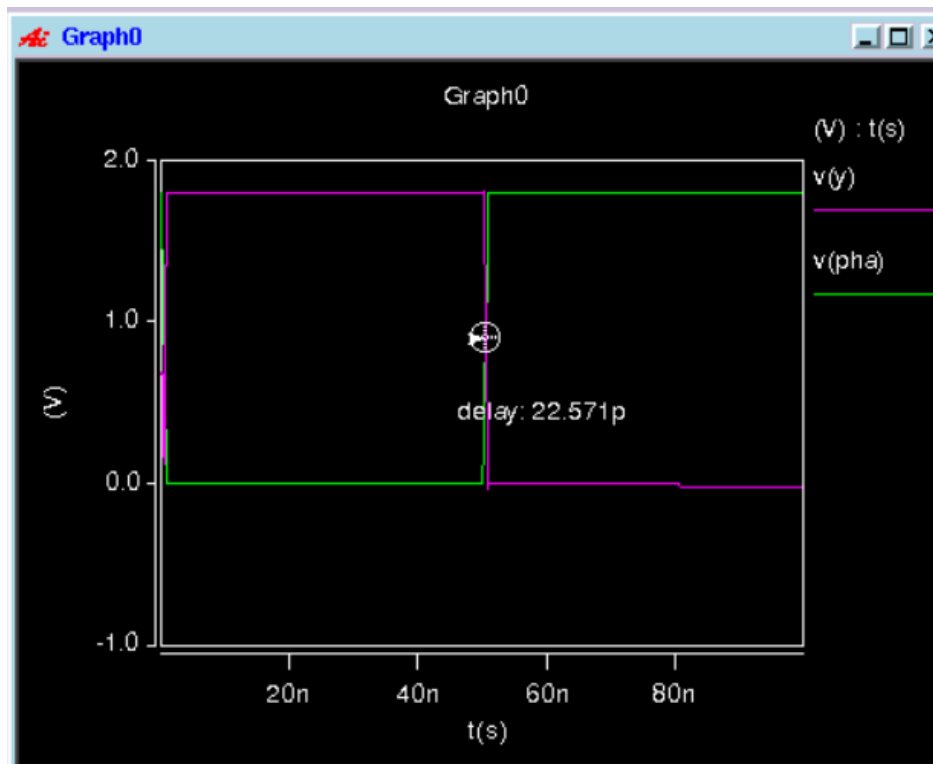

(iii) Questions of the labs:

1. Compare the DelayCin To Cout between 4-bit carry-ripple adder and 4-bit carry-skip adder, and explain the reason of the difference.

依照這次助教的測資比較，carry-ripple 較快，而使用 lab 測資則是 carry-skip 快。我覺得應該是這次只連了 4 顆 full adder，carry-skip 效果沒有很顯著，所以他們互有快慢，如果再串連更多 full adder，carry-skip 應該會較快。

2. Discuss what are the benefits using transmission gates to realize a 4:1 MUX, and explain the reasons.

transmission gates 最大的好處是可以減少 layout 的面積，相較於其他畫法使用較少的電晶體，而且 delay 也比較短。

3. What is "Monotonicity Problem" and how can we resolve this problem?

這個現象發生在 dynamic gate。如果在 pha 在 evaluate 的狀況下更動 inputA 的值(由 1->0)，output Y 理論上要馬上跟著更動，但是他沒有（如上面 dynamic inverter 圖示），而是到下一次 precharge 才改變值由 0->1，這個現象稱為 Monotonicity Problem。

To resolve the problem:we should follow dynamic stage with inverting static gate. The inverting static gate can help recharging the next dynamic stage During evaluation period.